

1. Consider a sinusoidal oscillator consisting of an amplifier having a frequency independent gain A (where A is positive) and a second order bandpass filter with a pole frequency ω_0 and a centre frequency gain K .
- Find the frequency of oscillation and the condition that A and K must satisfy for sustained oscillation.
 - Derive an expression for $\frac{d\phi}{d\omega}$, evaluated at $\omega = \omega_0$.
 - Use the result of (b) to find an expression for the per unit change in frequency of oscillation resulting from a phase angle change of $\Delta\phi$ in the amplifier transfer function.

2. An oscillator is formed by loading a transconductance amplifier having a positive gain with a parallel RLC circuit and connecting the output directly to the input (thus applying positive feedback with $\beta=1$). Let the transconductance amplifier have an input resistance of $10\text{K}\Omega$ and an output resistance of $10\text{K}\Omega$. The LC resonator has $L = 10\mu\text{H}$, $C = 1000\text{pF}$ and $Q = 100$. For what value of transconductance G_m will the circuit oscillate?

3. In an oscillator circuit, the frequency selective network exhibits a loss of 20 dB and a phase shift of 180° at ω_0 . What is the minimum gain and phase shift that the amplifier must have for oscillation to begin?

4. Consider the circuit in figure 1.

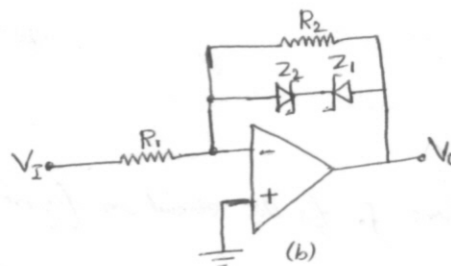
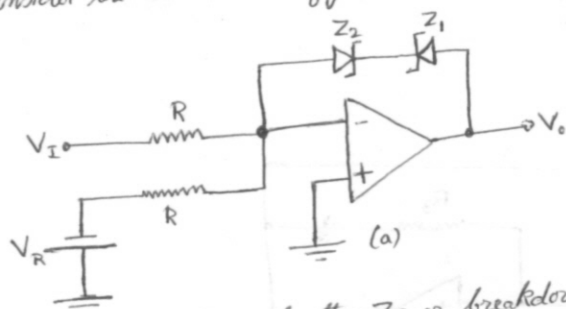


Figure 1

Let V_{Z1} and V_{Z2} be the Zener breakdown voltages of Zener diodes Z_1 and Z_2 respectively. Assume the diodes have a forward drop of 0.7V . Sketch and label the transfer characteristics of circuits in figure 1.

5. Consider an usual Wien bridge oscillator circuit. Show that its frequency selective feedback network is actually a bandpass filter. Find its frequency of oscillation and centre frequency gain.
6. Consider the circuit in figure 2. Find $L(s)$, $L(j\omega)$, frequency for zero loop phase, and R_2/R_1 for oscillation.

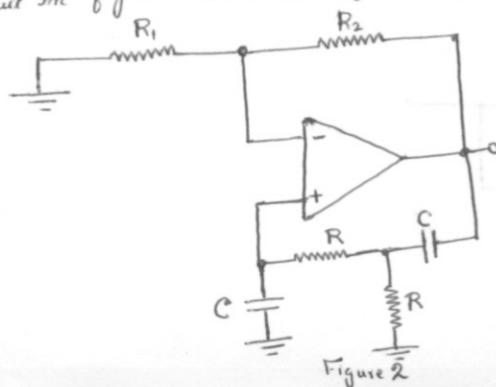


Figure 2

7. Calculate $L(s)$, $L(j\omega)$, frequency for zero loop-phase and R_2/R_1 for oscillation for the circuit in figure 3.

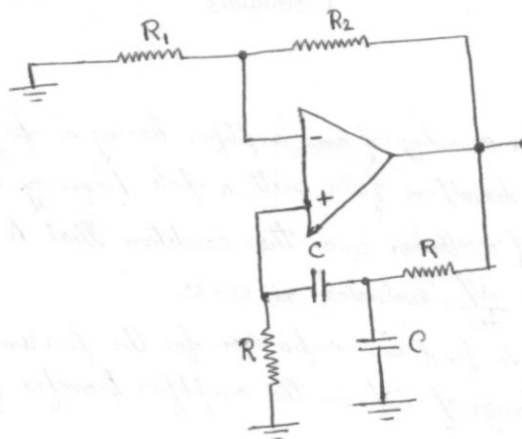


Figure 3

8. Consider the circuit in figure 4. Find V_x in terms of V_o . For $R = 10k\Omega$, find C and R_f to obtain sinusoidal oscillations at $10kHz$.

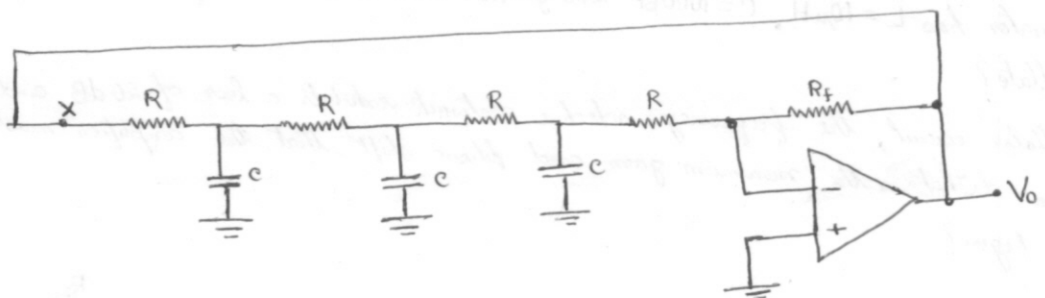


Figure 4

9. Determine f_o for the circuit in figure 5.

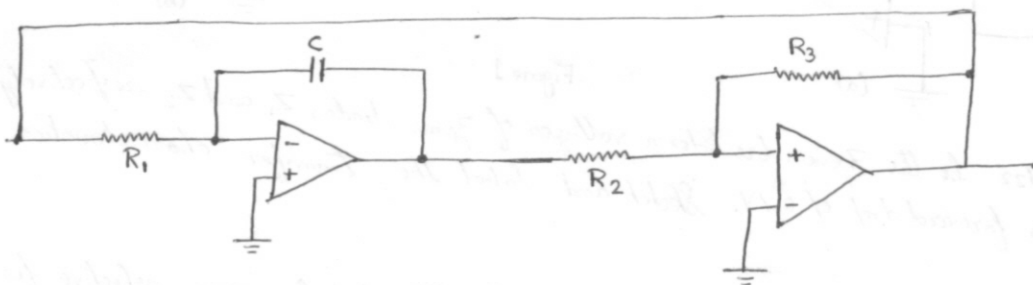


Figure 5.

10. Repeat problem 9 if $R_1 = R_2$.

11. Determine the frequency of oscillation of the circuit in figure 6.

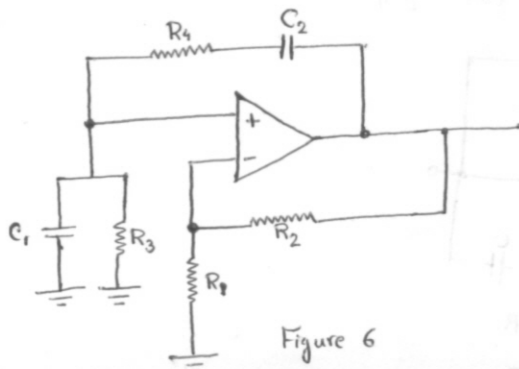


Figure 6

12. Design a phase shift oscillator so that $f_0 = 1 \text{ KHz}$.
13. Design a Wien bridge oscillator that will oscillate at 2 KHz .
14. Design a quadrature oscillator to operate at a frequency of 1.5 KHz .
15. Derive an expression for the frequency of oscillation of the circuit shown in figure 7. What is the ratio R_2/R_1 required for oscillation?

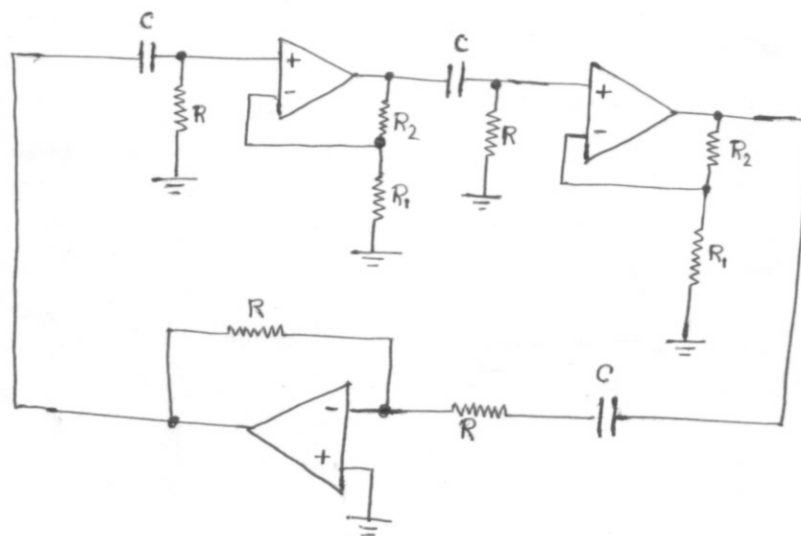


Figure 7

16. A crystal has a series resonant frequency of 10 MHz , series resistance of 40Ω , Q factor of 25000 , and parallel capacitance of 10 pF . (a) What are the values of L and C_s for this crystal? (b) What is the parallel resonant frequency of the crystal? (c) The crystal is placed in an oscillator circuit in parallel with a total capacitance of 22 pF . What will be the frequency of oscillation.