

## DIGITAL LOGIC AND PROCESSOR

### Experiment 9

### Microprogram Controller

Monsoon 2011

The execution of every instruction in a program, written and stored by the user in the Program Memory, is achieved by performing a sequence of steps, each step requiring specific hardware operations like data transfer, ALU operation, program flow control etc. The set of values of the control bits needed at any step by the various hardware blocks of the Processor defines a Microinstruction. The task of generating the correct sequence of Microinstructions constituting the Microprogram required for the execution of an Instruction is handled by the **Microprogram Controller**, consisting of the **Instruction Decoder**, the **Microsequencer** and the **Microprogram Memory**.

The process of execution of an instruction is initiated by the Fetch cycle, which consists of the following three steps, taking place at successive active edges of the Clock pulse.

- (i) Send the Instruction Address from PC to the Memory Address Register (MR):  $[MR] \leftarrow [PC]$ .
- (ii) Read the Op(erational) Code of the Instruction from the addressed Memory location and load it into the Instruction Register (IR):  $[IR] \leftarrow [[MR]]$ .
- (iii) Decode the Op Code (OC) by the Instruction Decoder to generate the Starting Address (SA) of the Microprogram for the Instruction to be executed, and load SA into the Microsequencer (MS), which provides the Microprogram Memory Address (MA) at its output:  $MA \leftarrow SA$ .

The output of the Microprogram Memory is connected to all the hardware blocks according to the control bits needed by them. Thus the Microinstruction given out by the Microprogram Memory in response to the address MA provides all the control action required at each step. Note that the Microprogram Memory, being a Read-Only Memory (ROM), does not require any Clock pulse and is thus combinational in nature. One can therefore design the Microprogram Memory using gates, as we will actually be doing in this experiment.

The Fetch cycle presupposes that the Address of the location where the Instruction has been stored in the Program Memory is available in the Program Counter (PC), and that the Microsequencer (MS) has been initialised to give  $MA = 000\dots00$ . The Fetch cycle is followed by the Execution cycle, which starts with the Microsequencer (MS) loaded to give  $MA = SA$ , and consists of as many steps as necessary for performing the task specified by the Instruction. As in the Fetch cycle, the Microinstruction given out by the Microprogram Memory in response to the address MA generated by the Microsequencer provides all the control action required at each step.


The values of the control bits  $R_{MS}$  and  $L_{MS}$  in each Microinstruction decide the flow of the Microprogram as follows:


If  $R_{MS} = 1$ ,  $MA \leftarrow 000\dots00$  at the next active edge of the Clock.

If  $L_{MS} = 1$ ,  $MA \leftarrow SA$  at the next active edge of the Clock.

In this experiment, we will design an elementary Microprogram Controller, capable of handling just four instructions  $I_0, I_1, I_2, I_3$ . The Instruction Decoder will thus receive a 2-bit Op Code  $OC_{1-0}$  and generate a 4-bit Microprogram Starting Address  $SA_{3-0}$ , which will be used by the Microsequencer to generate a 4-bit Microprogram Memory Address  $MA_{3-0}$  as shown in Fig. 9.1. Table 9.1 gives the Op Code assignments and the Microprogram Address assignments for the four instructions. The Fetch cycle, of course, must have the Microprogram Address assignment as shown in the table. As no other hardware block of the Processor like registers or ALU will be used, each Microinstruction will only consist of two bits –  $R_{MS}$  and  $L_{MS}$ . The main objective of this experiment will be to study how a Microprogram Controller controls the flow of microprograms by the control bits  $R_{MS}$  and  $L_{MS}$ .

CD4011(NAND) and CD4081 (AND) are similar

 

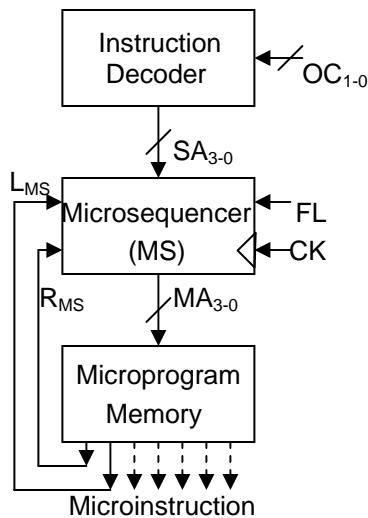

**Table 9.1 Microprogram Memory Map**

Instruction /Fetch Cycle	Op Code OC <sub>1-0</sub>	Microinstructions	Start Addr. SA <sub>3-0</sub>	End Address
a Fetch	-	3	0000	0010
b I <sub>0</sub>	00	4	0011	0110
c I <sub>1</sub>	01	3	0111	1001
d I <sub>2</sub>	10	2	1010	1011
e I <sub>3</sub>	11	4	1100	1111

**Fig. 9.1 Microprogram Controller**

1. The Microsequencer will have to be realised with the presettable counter CD4029, used earlier in Experiment 6. As this counter has a provision for presetting the count Q<sub>3-0</sub> to any value through the input D<sub>3-0</sub>, but no separate provision to clear the count to 0000, we will have to realise the functions of the control bits R<sub>MS</sub> and L<sub>MS</sub> by incorporating the following logic (taking FL = 0 always):

$$D_{3-0} = SA_{3-0} \text{ if } L_{MS} = 1, \text{ and } D_{3-0} = 0000 \text{ if } R_{MS} = 1; SEN = L_{MS} + R_{MS}.$$

Connect the counter control inputs CI', U/D' and B/D' to V<sub>CC</sub>/ Gnd appropriately to obtain a binary up counter. Design the necessary combinational logic circuits using 2-input NOR/NAND/AND gates.

2. Design the Instruction Decoder so that it satisfies the relationship between OC and SA given in Table 9.1. Obtain Boolean expressions for the four bits comprising SA<sub>3-0</sub> in terms of the Op Code bits OC<sub>1-0</sub> and realise them using 2-input NOR/NAND/AND gates.
3. Given that R<sub>MS</sub> = 1 only in the last Microinstruction of each Microprogram, and L<sub>MS</sub> = 1 only in the last Microinstruction of the Fetch cycle, construct the K-map for the two Microinstruction bits R<sub>MS</sub> and L<sub>MS</sub> in terms of MA<sub>3-0</sub>, and generate R<sub>MS</sub> and L<sub>MS</sub> using the two 4-input multiplexers available in the 74LS153 chip, used in Experiment 4. Use MA<sub>3</sub> and MA<sub>2</sub> as the Select inputs of the multiplexers and generate the multiplexer inputs from MA<sub>1</sub> and MA<sub>0</sub> with 2-input NOR/NAND/AND gates.
4. Decide on the final implementation of all the combinational circuits so that the complete circuit can be made using one each of the CD4001, CD4011 and CD4081 chips.
5. Assemble the complete circuit and connect MA<sub>3-0</sub>, R<sub>MS</sub> and L<sub>MS</sub> to LED Displays. Connect the Op Code input OC<sub>1-0</sub> to two Input Switches. Apply Manual Clock pulses to the Microsequencer Clock input and tabulate the sequence of MA<sub>3-0</sub>, R<sub>MS</sub> and L<sub>MS</sub> generated by the Microprogram Controller for each value of OC<sub>1-0</sub>, applied from the two input Switches. Verify that the observed sequence is according to Table 9.1.

