

1. A negative feedback amplifier has a closed loop gain $A_f = 100$ and an open loop gain $A = 10^5$. What is the feedback factor β ? If a manufacturing error results in a reduction of A to 10^3 , what closed loop gain results? What is the percentage change in A_f corresponding to this factor of 100 reduction in A ?

2. Consider the feedback amplifier configuration of figure 1. Assume the op-amp has infinite input resistance and zero output resistance. Calculate β . If $A = 100$, what is the closed loop gain? What is the gain in dB?

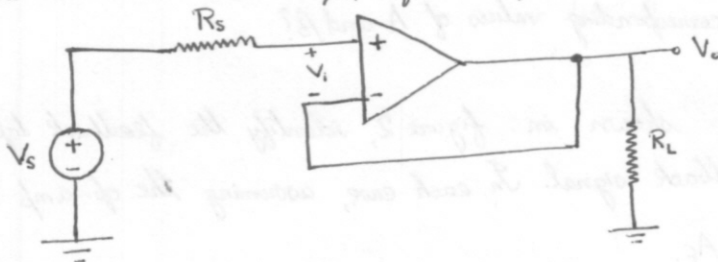


Figure 1

3. Consider the usual circuit configuration of a negative feedback amplifier. Find the relationship between A and β for which the sensitivity of closed loop gain to open loop gain — i.e. $(dA_f/A_f)/(dA/A)$ is -20dB . For what value of $A\beta$ does the sensitivity become $1/2$?
4. It is required to design an amplifier with a gain of 100 that is accurate to within $\pm 1\%$. You have available amplifier stages with a gain of 1000 that is accurate to within $\pm 30\%$. Provide a design that uses a number of these gain stages in cascade with each stage employing negative feedback of an appropriate amount.
5. In a feedback amplifier for which $A = 10^4$ and $A_f = 10^3$ what is the gain desensitivity factor? Find the gain A_f exactly and approximately when A drops by 10% and A drops by 40% .
6. A particular amplifier has a nonlinear transfer characteristic that can be approximated as follows:
- for small input signals, $|V_i| \leq 10\text{mV}$, $V_o/V_i = 10^3$
 - for intermediate input signals, $10\text{mV} \leq |V_i| \leq 50\text{mV}$, $V_o/V_i = 10^2$
 - for large input signals, $|V_i| \geq 50\text{mV}$, the output saturates. If the amplifier is connected in a negative feedback loop, find the feedback factor β that reduces the factor of 10 change in gain (occurring at $|V_i| = 10\text{mV}$) to only a 10% change. What is the transfer characteristic of the amplifier with feedback?
7. A series shunt feedback amplifier represented by the standard configuration uses an ideal basic voltage amplifier and operates with $V_s = 100\text{mV}$, $V_f = 90\text{mV}$ and $V_o = 10\text{V}$. Calculate A and β .

8. A shunt series feedback amplifier uses an ideal basic current amplifier and operates with $I_s = 100\mu\text{A}$, $I_f = 90\mu\text{A}$ and $I_o = 10\text{mA}$. Calculate A and β .
9. A series series feedback amplifier using an ideal transconductance amplifier operates with $V_s = 100\text{mV}$, $V_f = 95\text{mV}$ and $I_o = 10\text{mA}$. What are the corresponding values of A and β ?
10. A shunt shunt feedback amplifier using an ideal transresistance amplifier operates with $I_s = 100\mu\text{A}$, $I_f = 95\mu\text{A}$ and $V_o = 10\text{V}$. What are the corresponding values of A and β ?
11. For each of the op-amp circuits shown in figure 2, identify the feedback topology, the output variable being sampled and the feedback signal. In each case, assuming the op-amp to be ideal, find an expression for β and hence A_f .

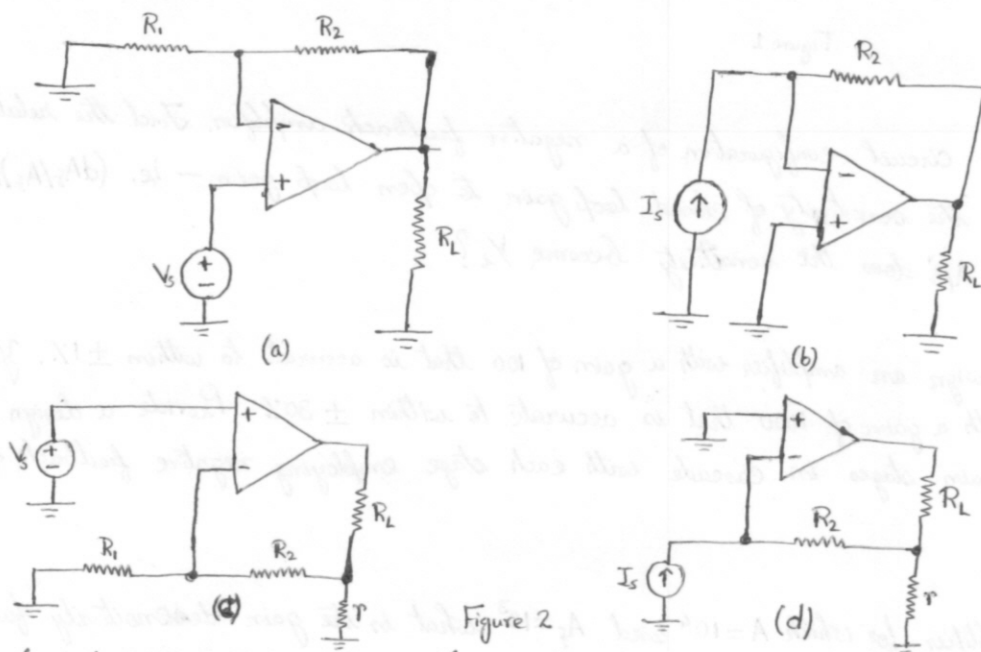


Figure 2

12. A series shunt feedback amplifier employs a basic amplifier with input and output resistances each of $1\text{k}\Omega$ and gain $A = 1000\text{V/V}$. The feedback factor $\beta = 0.1\text{V/V}$. Find the gain A_f , input resistance R_i , and the output resistance R_o of the closed loop amplifier.
13. A series shunt feedback circuit employs a basic voltage amplifier that has a dc gain of 10^4V/V and an STC frequency response with a unity-gain frequency of 1MHz . The input resistance of the basic amplifier is $10\text{k}\Omega$ and its output resistance is $1\text{k}\Omega$. If the feedback factor $\beta = 0.1\text{V/V}$, find the input impedance Z_i and the output impedance Z_o of the feedback amplifier. Give equivalent circuit representations of these impedances. Also find the value of each impedance at 10^3Hz and at 10^5Hz .
14. A feedback amplifier utilizing voltage sampling and employing a basic voltage amplifier with a gain of 100 and an output resistance of 1000Ω has a closed loop output resistance of 100Ω . What is the closed loop gain? If the basic amplifier is used to implement a unity gain voltage buffer, what output resistance do you expect?

15. A series-series feedback amplifier employs a transconductance amplifier having $G_m = 100 \text{ mA/V}$, input resistance of $10 \text{ k}\Omega$ and output resistance of $100 \text{ k}\Omega$. The feedback network has $\beta = 0.1 \text{ V/mA}$, an input resistance (with port 1 open circuited) of 100Ω , and an input resistance (with port 2 open circuited) of $10 \text{ k}\Omega$. The amplifier operates with a signal source having a resistance of $10 \text{ k}\Omega$ and with a load resistance of $10 \text{ k}\Omega$. Find A_f , R_{in} and R_{out} .

16. A transresistance amplifier having an open circuit "gain" of 100 V/mA , an input resistance of $1 \text{ k}\Omega$, and an output resistance of $1 \text{ k}\Omega$ is connected in a negative feedback loop employing a shunt-shunt topology. The feedback network has an input resistance (with port 1 short circuited) of $10 \text{ k}\Omega$ and an input resistance (with port 2 short circuited) of $10 \text{ k}\Omega$ and provides a feedback factor $\beta = 0.1 \text{ mA/V}$. The amplifier is fed with a current source having $R_s = 10 \text{ k}\Omega$, and a load resistance $R_L = 1 \text{ k}\Omega$ is connected at the output. Find the transresistance A_f of the feedback amplifier, its input resistance R_{in} and its output resistance R_{out} .

17. Negative feedback is to be used to modify the characteristics of a particular amplifier for various purposes. Identify the feedback topology to be used if:

- (a) Input resistance is to be lowered and output resistance raised.
- (b) Both input and output resistances are to be raised.
- (c) Both input and output resistances are to be lowered.

18. Consider the circuit in figure 3. Use the feedback method to find the voltage gain V_o/V_s , the input resistance R_{in} and the output resistance R_{out} . The op-amp has open loop gain $\mu = 10^4 \text{ V/V}$, $R_{id} = 100 \text{ k}\Omega$ and $r_o = 1 \text{ k}\Omega$.

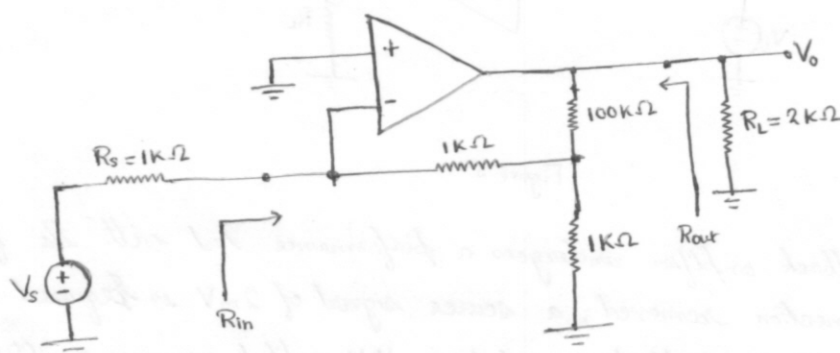


Figure 3

19. A current amplifier with a short circuit current gain of 100 A/A , an input resistance of $1 \text{ k}\Omega$ and an output resistance of $10 \text{ k}\Omega$ is connected in a negative feedback loop employing the shunt series topology. The feedback network provides a feedback factor $\beta = 0.1 \text{ A/A}$. Lacking complete data about the situation, estimate the current gain, input resistance and output resistance of the feedback amplifier.

20. Figure 4 shows how a shunt series feedback amplifier can be employed to design a current amplifier using op-amp.

(a) Show that for large loop gain, the current gain is approximately given by $\frac{I_o}{I_s} \approx 1 + \frac{R_f}{r}$.

(b) Find the closed loop gain I_o/I_s , the input resistance (excluding R_s), and the output resistance (excluding R_L) for the case: open loop voltage gain of op-amp = 10^4 V/V, $R_{id} = 100\text{k}\Omega$, op-amp output resistance = $1\text{k}\Omega$, $R_s = R_L = 10\text{k}\Omega$, $r = 100\Omega$ and $R_f = 1\text{k}\Omega$.

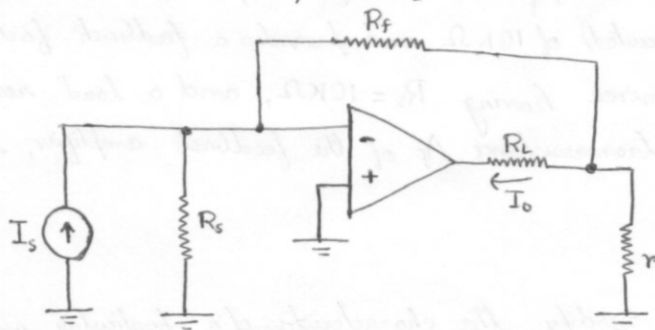


Figure 4

21. Consider the circuit in figure 5. Show that, if the loop gain is large, the voltage gain is approximately given by $\frac{V_o}{V_s} \approx -\frac{R_f}{R_s}$.

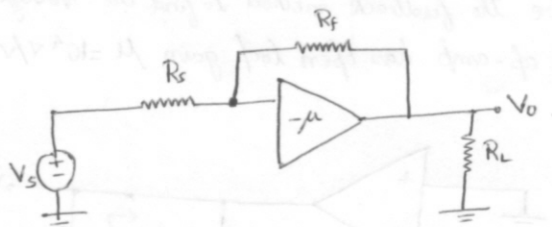


Figure 5

22. A newly constructed feedback amplifier undergoes a performance test with the following results: With the feedback connection removed, a source signal of 2mV is required to provide a 10V output to the load; with the feedback connected, a 10V output requires a 200mV source signal. For this amplifier, identify values of A , β , $A\beta$, the closed loop gain and the amount of feedback (in dB).